

EX. NO: 03

DATE : 19/09/2024

ENCODERS AND DECODERS

AIM: To simulate encoders and decoders in behavior, structural, and dataflow model of Verilog HDL.

SOFTWARE USED: Xilinx Vivado

HARDWARE USED: Basys3 FPGA Board

ENCODERS:

VERILOG HDL CODES:

4 to 2 line Encoder in Behavioral Model:

```
module encoder4to2_behav(D,Q);
input [3:0] D;
output reg [1:0] Q;
always@(*)
begin
if (D==4'b0001)
begin Q=2'b00; end
else if (D==4'b0010)
begin Q=2'b01; end
else if (D==4'b0100)
begin Q=2'b10; end
else if (D==4'b1000)
begin Q=2'b11; end
else
begin Q=2'b00; end
end
endmodule
```

4 to 2 line Encoder in Structural Model:

```
module encoder4to2_struct(D,Q );
input [3:0] D;
output[1:0] Q;
or (Q[0],D[1],D[3]);
or (Q[1],D[2],D[3]);
endmodule
```

4 to 2 line Encoder in Data flow model:

```
module encoder4to2_data(D,Q );
input [3:0] D;
output[1:0] Q;
assign Q[0]=D[1] | D[3];
assign Q[1]=D[2] | D[3];
endmodule
```

Test bench 4 to 2 line Encoder:

```
module tb_encoder4to2;
reg [3:0] D;
wire [1:0] Q;
//encoder4to2_data EN1(D,Q);
encoder4to2_struct EN2(D,Q);
//encoder4to2_behav EN3(D,Q);
initial
begin
    D=4'b0001;
    #10 D=4'b0010;
    #10 D=4'b0100;
    #10 D=4'b1000;
    #10 D=4'b0000;
    #10 $stop;
end
initial begin
    $monitor(" D = %b, Q = %b",D,Q);
end
endmodule
```

8 to 3 line Encoder:

```
module encoder8to3(D,Q);
input [7:0] D;
output[2:0] Q;
or (Q[0],D[1],D[3],D[5],D[7]);
or (Q[1],D[2],D[3],D[6],D[7]);
or (Q[2],D[4],D[5],D[6],D[7]);
endmodule
```

Test bench for 8 to 3 line Encoder:

```
module tb_encoder8to3;
reg [7:0] D;
wire [2:0] Q;
encoder8to3 EN3(D,Q);
initial
begin
    D=8'b00000001;
    #10 D=8'b00000010;
    #10 D=8'b00000100;
    #10 D=8'b00001000;
    #10 D=8'b00010000;
    #10 D=8'b00100000;
    #10 D=8'b01000000;
    #10 D=8'b10000000;
    #10 $stop;
end
initial begin
    $monitor(" D = %b, Q = %b",D,Q);
end
endmodule
```

8 to 3 Priority Encoder:

```
module encoder8to3_priority(D, Q);
    input [7:0] D;
    output reg [2:0] Q;


    always @(*) begin
        if (D[7]==1) Q=3'b111;
        else if (D[6]==1) Q=3'b110;
        else if (D[5]==1) Q=3'b101;
        else if (D[4]==1) Q=3'b100;
        else if (D[3]==1) Q=3'b011;
        else if (D[2]==1) Q=3'b010;
        else if (D[1]==1) Q=3'b001;
        else if (D[0]==1) Q=3'b000;
        else
            Q=3'bxxx;
    end
endmodule
```

Testbench for 8 to 3 Priority Encoder:


```
module tb_encoder8to3_priority;
    reg [7:0] D;
    wire [2:0] Q;
    encoder8to3_priority EN3(D,Q);
    initial
    begin
        D=8'b00000001;
        #10 D=8'b00000010;
        #10 D=8'b00000100;
        #10 D=8'b00001000;
        #10 D=8'b00010000;
        #10 D=8'b00100000;
        #10 D=8'b01000000;
        #10 D=8'b10000000;
        #10 D=8'b00000001;
        #10 D=8'b00000011;
        #10 D=8'b00000111;
        #10 D=8'b00001111;
        #10 D=8'b00011111;
        #10 D=8'b00111111;
        #10 D=8'b01111111;
        #10 D=8'b11111111;
        #10 $stop;
    end
    initial begin
        $monitor(" D = %b, Q = %b",D,Q);
    end
endmodule
```

SIMULATION WAVEFORMS:


4 to 2 line Encoder in Behavioral Model:

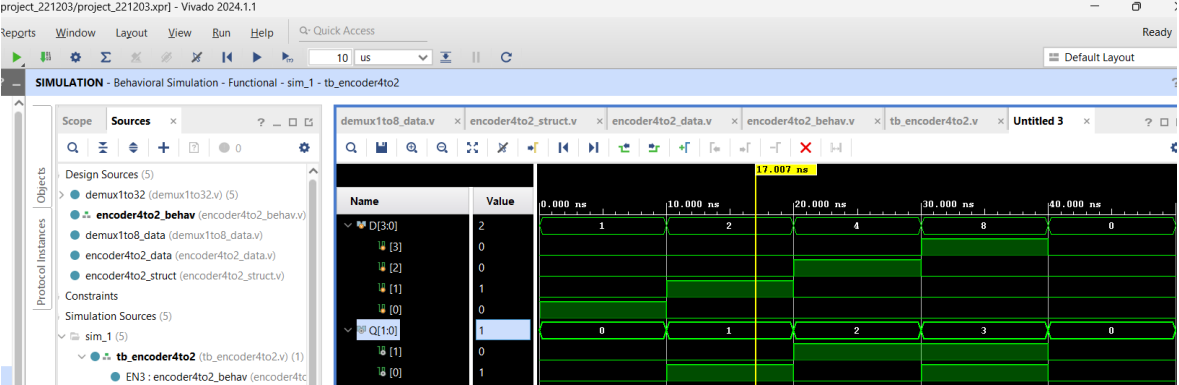


4 to 2 line Encoder in Structural Model:

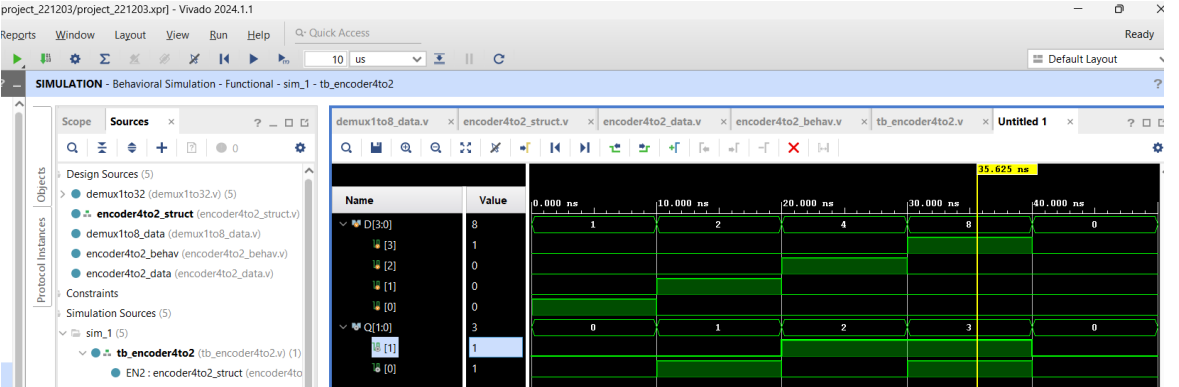


4 to 2 line Encoder in Data flow model:

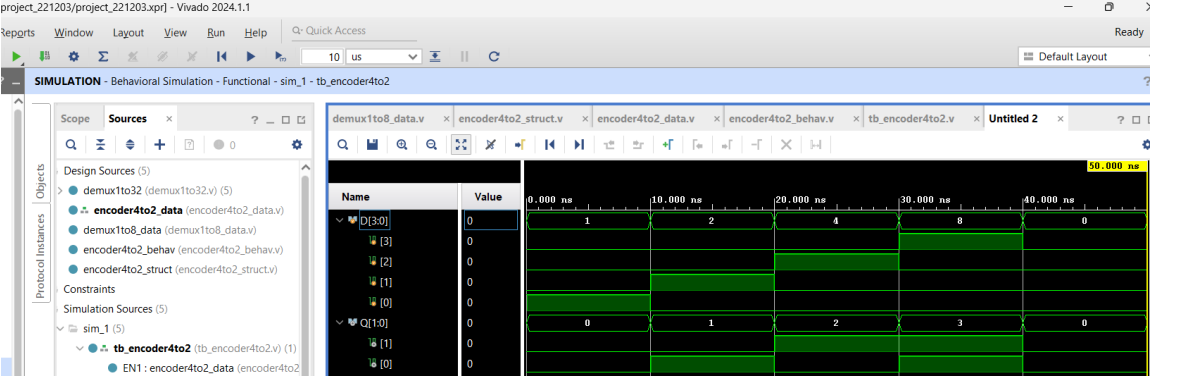

8 to 3 line Encoder:

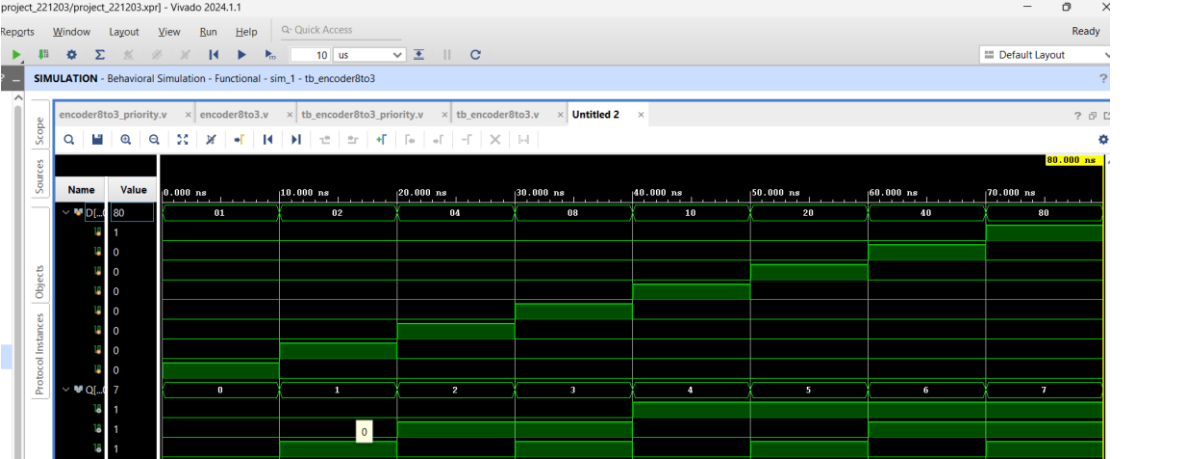

8 to 3 Priority Encoder:

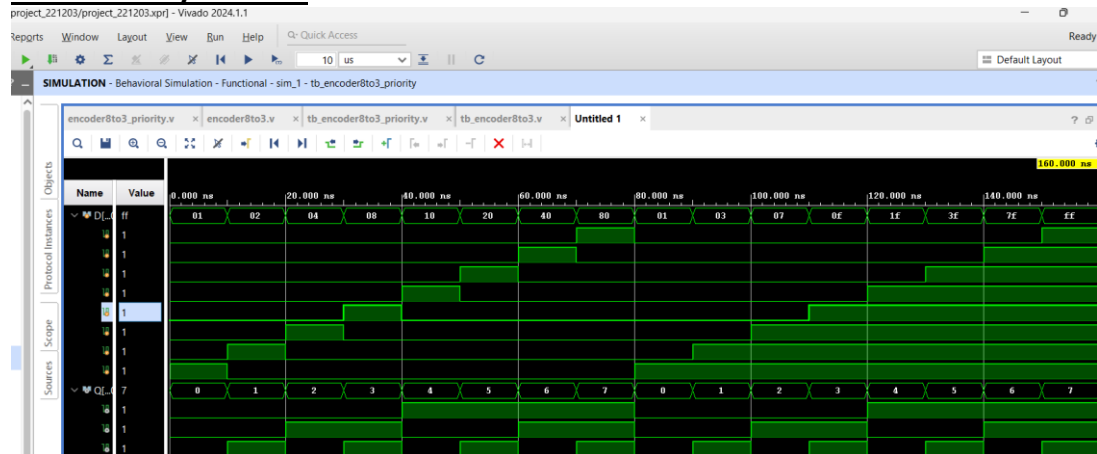

HARDWARE OUTPUT:

4 to 2 line Encoder:

I/O ports:

Inputs:

D[3]: R2

D[2]: T1

D[1]: U1


D[0]: W2

Outputs:

Q[1]: L1

Q[0]: P1

For D[3]=1, D[2]=0, D[1]=0, D[0]=0

 

8 to 3 line Encoder:

I/O ports:

Inputs:


D{7}: R2
D[6]: T1
D[5]: U1
D[4]: W2

D[3]: R3
D[2]: T2
D[1]: T3
D[0]: V2

Outputs:

Q[2]: L1
Q[1]: P1
Q[0]: N3

 For D[7]=1, D[6]=0, D[5]=0, D[4]=0
D[3]=0, D[2]=0, D[1]=0, D[0]=0



8 to 3 Priority Encoder:

Inputs:


D{7}: R2
D[6]: T1
D[5]: U1
D[4]: W2

D[3]: R3
D[2]: T2
D[1]: T3
D[0]: V2

Outputs:


Q[2]: L1
Q[1]: P1
Q[0]: N3

 For D[7]=0, D[6]=0, D[5]=1, D[4]=1
D[3]=1, D[2]=1, D[1]=1, D[0]=1



TRUTH TABLES AND CIRCUIT DIAGRAMS:

4 to 2 line Encoder:

 

Inputs				Outputs	
D ₃	D ₂	D ₁	D ₀	Q ₁	Q ₀
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1
0	0	0	0	x	x

$$Q_1 = \sim D_0 \& \sim D_1 \& (D_2 \wedge D_3)$$

$$Q_0 = \sim D_0 \& \sim D_3 \& (D_2 \wedge D_1)$$

$$Q_1 = D_2 \mid D_3$$

$$Q_0 = D_1 \mid D_3$$

 


Fig. 4to2 line decoder

8 to 3 line Encoder:



INPUTS								OUTPUTS		
Y7	Y6	Y5	Y4	Y3	Y2	Y1	Y0	A2	A1	A0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

 



Fig. 8to3 line encoder

$$A_2 = Y_4 + Y_5 + Y_6 + Y_7$$

$$A_1 = Y_2 + Y_3 + Y_6 + Y_7$$

$$A_0 = Y_7 + Y_5 + Y_3 + Y_1$$

8 to 3 Priority Encoder:

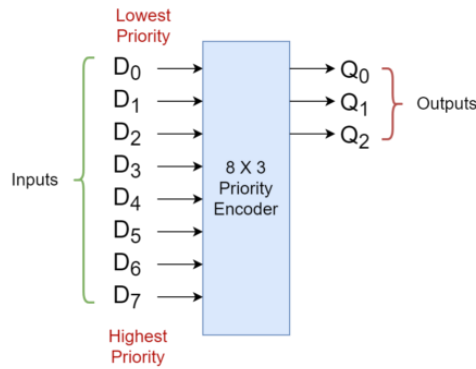

Inputs								Outputs		
D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	Q ₂	Q ₁	Q ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	x	0	0	1
0	0	0	0	0	1	x	x	0	1	0
0	0	0	0	1	x	x	x	0	1	1
0	0	0	1	x	x	x	x	1	0	0
0	0	1	x	x	x	x	x	1	0	1
0	1	x	x	x	x	x	x	1	1	0
1	x	x	x	x	x	x	x	1	1	1

X = Don't Care

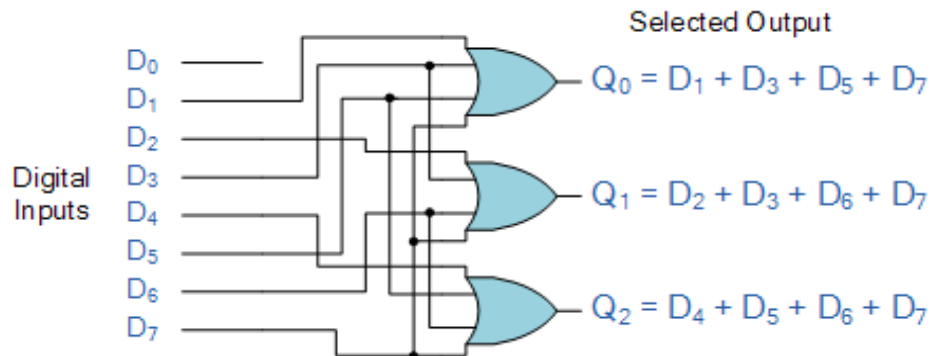


Fig. 8to3 priority encoder

DECODERS:

VERILOG HDL CODES:

2 to 4 Decoder in Behavioral Model:

```
module decoder2to4_behav(A, Y);
    input [1:0] A;
    output reg [3:0] Y;
    always @(*) begin
        Y = 4'b0000; // Default
        case (A)
            2'b00: Y[0] = 1;
            2'b01: Y[1] = 1;
            2'b10: Y[2] = 1;
            2'b11: Y[3] = 1;
        endcase
    end
endmodule
```

2 to 4 Decoder in Dataflow Model:

```
module decoder2to4_data(A, Y);
    input [1:0] A;
    output [3:0] Y;
    assign Y[0] = ~A[1] & ~A[0];
    assign Y[1] = ~A[1] & A[0];
    assign Y[2] = A[1] & ~A[0];
    assign Y[3] = A[1] & A[0];
endmodule
```

2 to 4 Decoder in Structural Model:

```
module decoder2to4_struct(A, Y);
    input [1:0] A;
    output [3:0] Y;
    wire not_A0, not_A1;
    not (not_A0, A[0]);
    not (not_A1, A[1]);
    and (Y[0], not_A0, not_A1);
    and (Y[1], A[0], not_A1);
    and (Y[2], not_A0, A[1]);
    and (Y[3], A[0], A[1]);
endmodule
```


Test Bench for 2 to 4 Decoder:

```
module tb_decoder2to4;
    reg [1:0] A;
    wire [3:0] Y;
    decoder2to4_behav DC1(A, Y);
    //decoder2to4_data DC2(A, Y);
    //decoder2to4_struct DC3(A, Y);
    initial begin
        A = 2'b00; #10;
        A = 2'b01; #10;
        A = 2'b10; #10;
        A = 2'b11; #10;
        $stop;
    end
    initial begin
        $monitor("A = %b, Y = %b", A, Y);
    end
endmodule
```

3 to 8 Decoder:

```
module decoder3to8_behav(A, Y);
    input [2:0] A;
    output reg [7:0] Y;
    always @(*) begin
        Y = 8'b00000000; // Default
        case (A)
            3'b000: Y[0] = 1;
            3'b001: Y[1] = 1;
            3'b010: Y[2] = 1;
            3'b011: Y[3] = 1;
            3'b100: Y[4] = 1;
            3'b101: Y[5] = 1;
            3'b110: Y[6] = 1;
            3'b111: Y[7] = 1;
        endcase
    end
endmodule
```

Test Bench for 3 to 8 Decoder:

```
module tb_decoder3to8;
    reg [2:0] A;
    wire [7:0] Y;
    decoder3to8_behav DC(A, Y);
    initial begin
        A = 3'b000; #10;
        A = 3'b001; #10;
        A = 3'b010; #10;
        A = 3'b011; #10;
        A = 3'b100; #10;
        A = 3'b101; #10;
        A = 3'b110; #10;
    end
endmodule
```

```

    A = 3'b111; #10;
    $stop;
end
initial begin
    $monitor("A = %b, Y = %b", A, Y);
end
endmodule

```

5 to 32 line decoder using 2 to 4 line Decoder and 3 to 8 line decoders:

```

module decoder5to32(A,Y,enable);
    input [4:0] A;
    input enable;
    output [31:0] Y;
    wire [3:0] E;
    decoder2to4 D0 (A[4:3],E,enable);
    decoder3to8 D1(A[2:0],Y[7:0],E[0]);
    decoder3to8 D2(A[2:0],Y[15:8],E[1]);
    decoder3to8 D3(A[2:0],Y[23:16],E[2]);
    decoder3to8 D4(A[2:0],Y[31:24],E[3]);
endmodule

```

```

module decoder2to4(A, E, enable);
    input [1:0] A;
    input enable;
    output reg [3:0] E;
    always @(*) begin
        if (enable==1) begin
            case (A)
                2'b00: E = 4'b0001;
                2'b01: E = 4'b0010;
                2'b10: E = 4'b0100;
                2'b11: E = 4'b1000;
                default: E = 4'b0000;
            endcase
        end else
            E = 4'b0000;
        end
    end
endmodule

```

```

module decoder3to8(A, Y, enable);
    input [2:0] A;
    input enable;
    output reg [7:0] Y;
    always @(*) begin
        if (enable==1) begin
            case (A)
                3'b000: Y = 8'b00000001;
                3'b001: Y = 8'b00000010;
                3'b010: Y = 8'b00000100;
                3'b011: Y = 8'b00001000;
                3'b100: Y = 8'b00010000;
                3'b101: Y = 8'b00100000;
            endcase
        end
    end
endmodule

```

```

        3'b110: Y = 8'b01000000;
        3'b111: Y = 8'b10000000;
        default: Y = 8'b00000000;
    endcase
end else
    Y = 8'b00000000;
end
endmodule

```

Test Bench for 5 to 32 Decoder:


```

module tb_decoder5to32;
    reg [4:0] A;
    wire [31:0] Y;
    reg enable;
    decoder5to32 DC (A,Y,enable);
    initial begin
        $monitor("A = %b, Y = %b,enable = %b", A, Y,enable);
        enable=1'b1;
        for (integer i = 0; i < 32; i = i + 1) begin
            A = i;
            #10;
        end
        enable = 1'b0;
        #10 A=5'b000101;
        $finish;
    end
endmodule


```

SIMULATION WAVEFORMS:

2 to 4 Decoder in Behavioral Model:

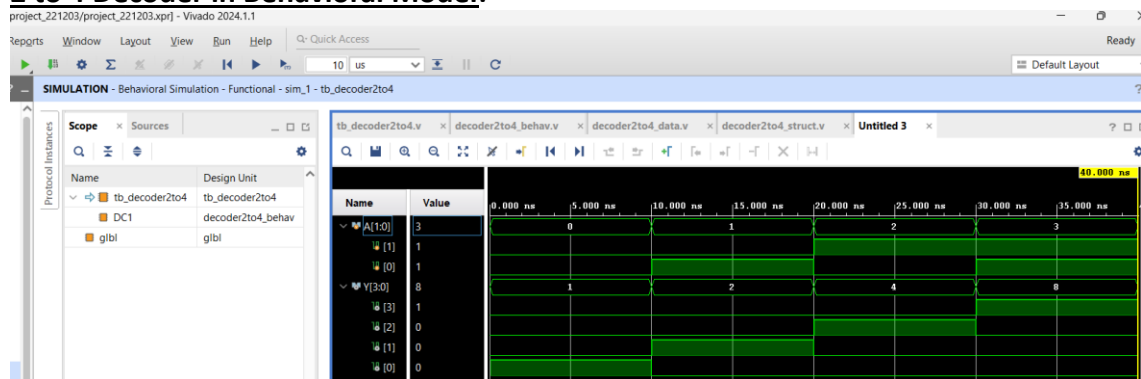


2 to 4 Decoder in Dataflow Model:

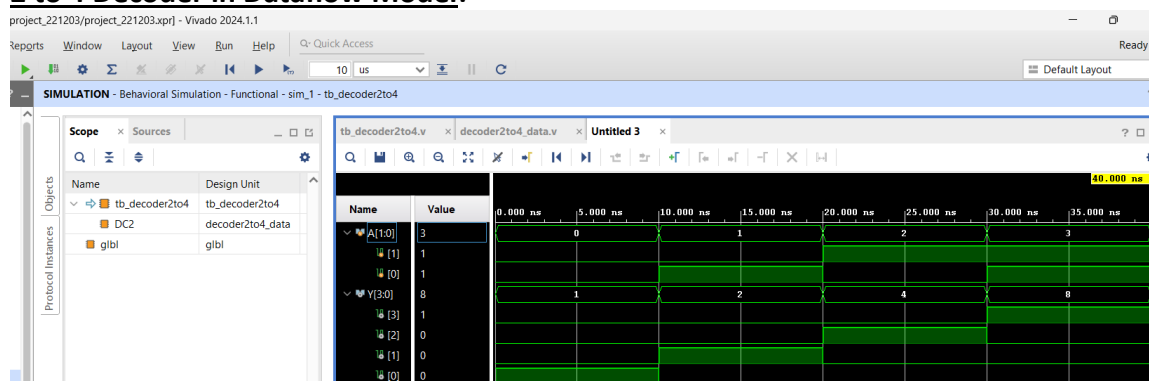


2 to 4 Decoder in Structural Model:

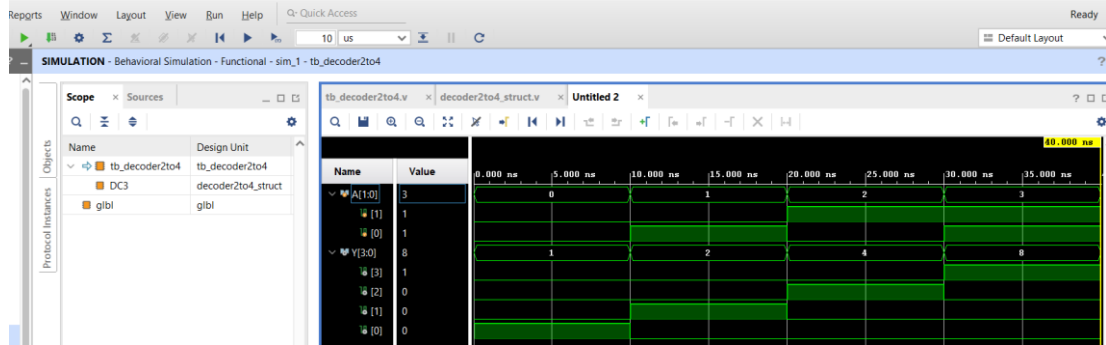project_221203/project_221203.xprj - Vivado 2024.1.1




3 to 8 Decoder:

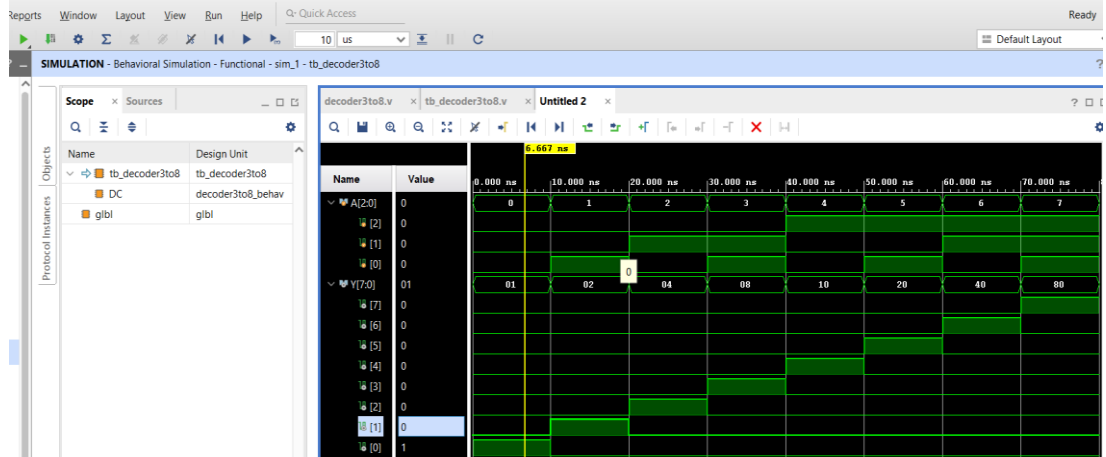project_221203/project_221203.xprj - Vivado 2024.1.1



5 to 32 line decoder:

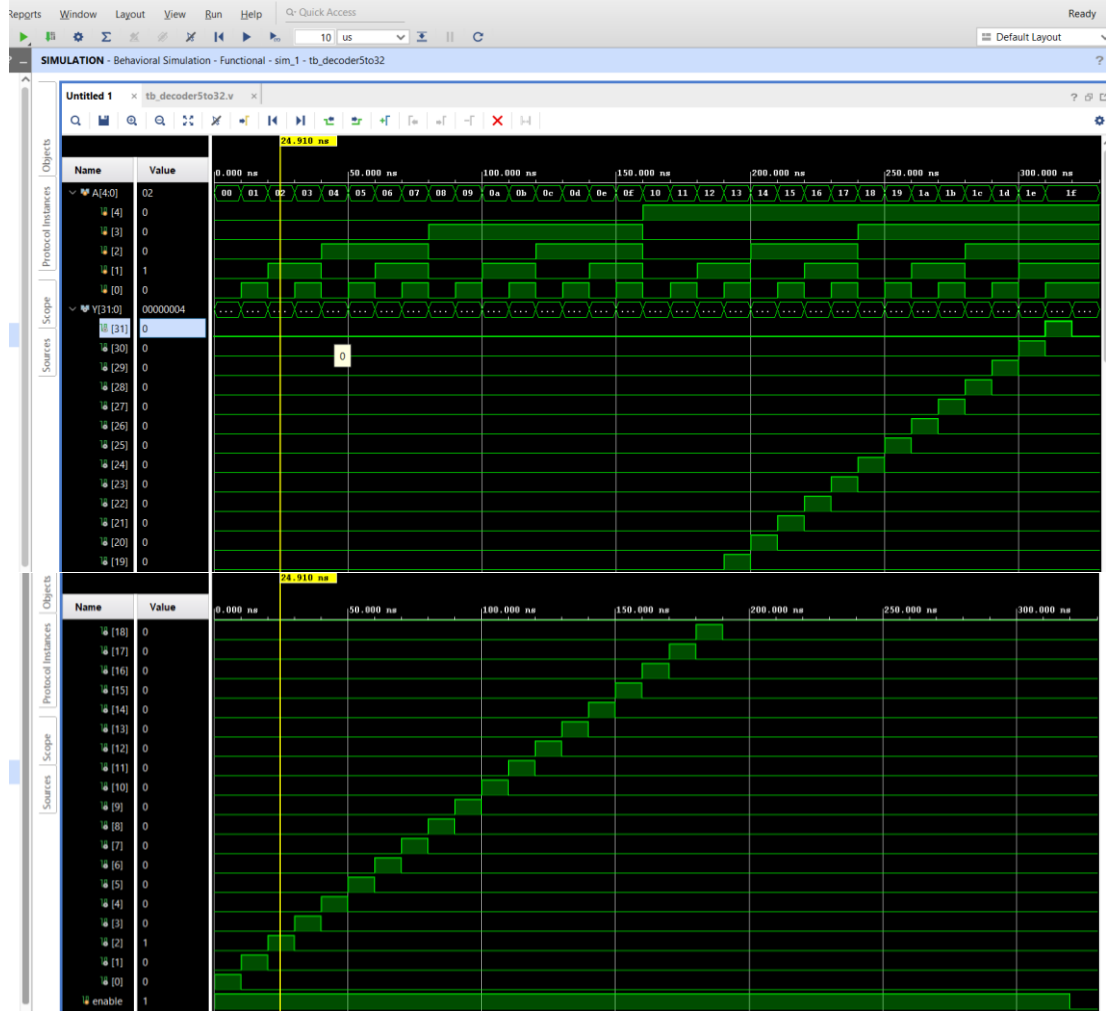project_221203/project_221203.xprj - Vivado 2024.1.1



HARDWARE OUTPUT:

2 to 4 Decoder :

I/O ports:

Inputs:

A[1]: R2

A[0]: T1

Outputs:


Y[3]: P1

Y[2]: N3

Y[1]: P3

Y[0]: U3

For A[1]=1, A[0]=0

 

3 to 8 Decoder:

I/O ports:

Inputs:

A[2]: R2

A[1]: T1

A[0]: U1

Outputs:

Y[7]: L1

Y[6]: P1

Y[5]: N3

Y[4]: P3


Y[3]: U3

Y[2]: W3

Y[1]: V3



Y[0]: V13

For A[2]=0, A[1]=0, A[0]=1

 

TRUTH TABLES AND CIRCUIT DIAGRAMS:

2 to 4 Decoder:

 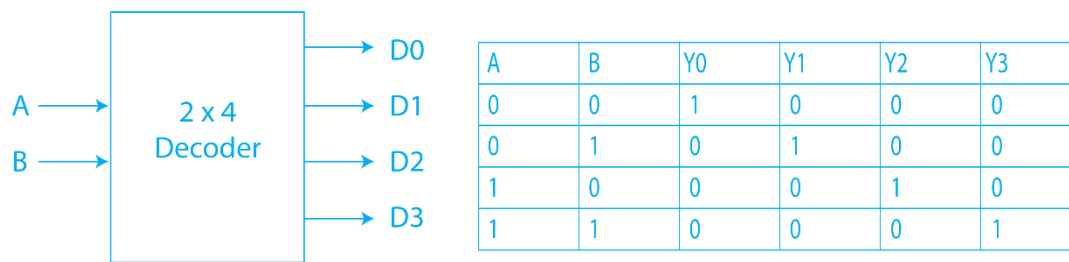

$$D_0 = A_0' A_1'$$


$$D_1 = A_1' A_0$$

$$D_2 = A_1 A_0'$$

$$D_3 = A_1 A_0$$

Fig. 2 to 4 Decoder

3 to 8 Decoder:

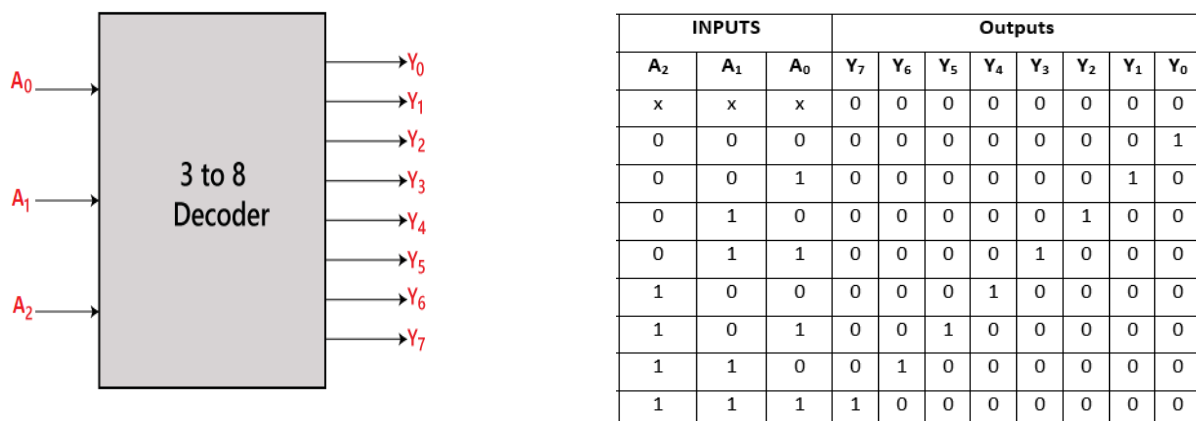

 


Fig. 3 to 8 Decoder

$$Y_0 = A_2' A_1' A_0'$$

$$Y_1 = A_2' A_1' A_0$$

$$Y_2 = A_2' A_1 A_0'$$

$$Y_3 = A_2' A_1 A_0$$


$$Y_4 = A_2 A_1' A_0'$$

$$Y_5 = A_2 A_1' A_0$$

$$Y_6 = A_2 A_1 A_0'$$

$$Y_7 = A_2 A_1 A_0$$

5 to 32 line decoder:

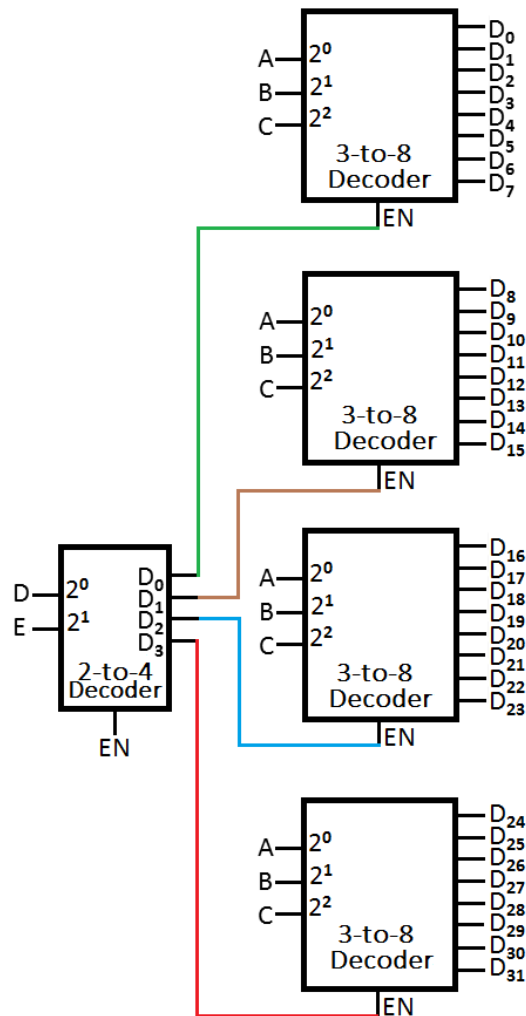

RESULT:

Thus, encoders and decoders were successfully implemented in Verilog HDL using behavioral, structural, and dataflow modeling. Their functionalities were verified through simulation using Xilinx Vivado software on the Basys3 FPGA board.