

EX. NO: 06

DATE : 11/10/2024

RANDOM ACCESS MEMORY

AIM: To design and Implement the RAM with 1 Kbyte of memory using Verilog HDL.

SOFTWARE USED: Xilinx Vivado

HARDWARE USED: Basys3 FPGA Board

RAM:

Verilog HDL Code:

```
module ram(  
    input clk,  
    input write_enable,  
    input [9:0] address,  
    input [7:0] data_in,  
    output reg [7:0] data_out  
);  
reg [7:0] ram_block[0:1023];  
always @(posedge clk) begin  
    if (write_enable) begin  
        ram_block[address] <= data_in; // Write data to RAM  
    end else begin  
        data_out <= ram_block[address]; // Read data from RAM  
    end  
end  
endmodule
```

Test bench for RAM:


```
module tb_ram;  
    reg clk;  
    reg write_enable;  
    reg [9:0] address;  
    reg [7:0] data_in;  
    wire [7:0] data_out;  
    ram AA(  
        .clk(clk),  
        .write_enable(write_enable),  
        .address(address),  
        .data_in(data_in),  
        .data_out(data_out)  
    );  
    always #5 clk = ~clk;  
    initial begin  
        clk = 1;
```

```

write_enable = 0;
address = 0;
data_in = 0;
#10 write_enable = 1; address = 10; data_in = 8'hAA;
#10 write_enable = 0; address = 10;
#10 if (data_out !== 8'hAA) $display("Error: data_out = %h", data_out);
#10 write_enable = 1; address = 20; data_in = 8'hBB;
#10 write_enable = 0; address = 20;
#10 if (data_out !== 8'hBB) $display("Error: data_out = %h", data_out);
#10 write_enable = 1; address = 30; data_in = 8'hCC;
#10 write_enable = 0; address = 30;
#10 if (data_out !== 8'hCC) $display("Error: data_out = %h", data_out);
#10 $finish;
end
initial begin
$monitor("clk=%b,write_enable=%b,address=%b,data_in=%b,data_out=%b",
clk,write_enable,address,data_in,data_out);
end
endmodule

```

SIMULATION WAVEFORM:

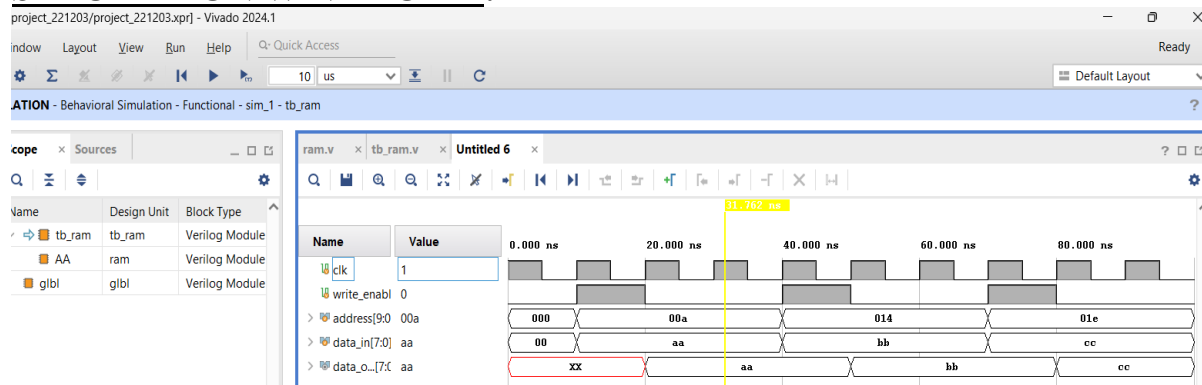

HARDWARE OUTPUT:

I/O ports:

Inputs:

data_in[7]: T1
data_in[6]: U1
data_in[5]: W2
data_in[4]: R3
data_in[3]: T2
data_in[2]: T3
data_in[1]: V2
data_in[0]: W13
clk: W5
write_enable: R2

address[9]: W14
address[8]: V15
address[7]: W15
address[6]: W17
address[5]: W16
address[4]: V16
address[3]: V17
address[2]: T18
address[1]: T17
address[0]: U18

Outputs:

data_out[7]: L1
data_out [6]: P1
data_out [5]: N3
data_out [4]: P3
data_out [3]: U3
data_out [2]: W3
data_out [1]: V3
data_out [0]: V13


For data_in[7] = 1
 data_in[6] = 1
 data_in[5] = 1
 data_in[4] = 0
 data_in[3] = 0
 data_in[2] = 0
 data_in[1] = 0
 data_in[0] = 0
 clk = 1
 write_enable = 1

address[9] = 0
 address[8] = 0
 address[7] = 0
 address[6] = 0
 address[5] = 1
 address[4] = 1
 address[3] = 1
 address[2] = 0
 address[1] = 0
 address[0] = 0


Output:

Previously stored data as output(since write_enable is in active state):

 data_out [7]=1, data_out [6]=1, data_out [5]=1, data_out [4]=1,
 data_out [3]=0, data_out [2]=0, data_out [1]=0, data_out [0]=0



CIRCUIT DIAGRAM:

 

RESULT:

The RAM has been successfully designed and implemented using Verilog HDL, and its functionalities have been thoroughly verified through simulation with Xilinx Vivado software on the Basys3 FPGA board.