

EX. NO: 04

DATE : 27/09/2024

## FLIP-FLOPS

**AIM:** To implement flipflops in Verilog HDL and verify their functionalities through behavioral simulation.

**SOFTWARE USED:** Xilinx Vivado

**HARDWARE USED:** Basys3 FPGA Board

**ADDERS:**

### **VERILOG HDL CODE:**

#### **SR flipflop:**

```
module sr_flipflop(s,r,clk,rst,q,qbar);
input s,r,clk,rst;
output reg q,qbar;
always @ (posedge clk)
begin

    if (rst==0)
        begin
            case ({s,r})
                2'b00: q=q;
                2'b01: q=1'b0;
                2'b10: q=1'b1;
                2'b11: q=1'bx; //Invalid
            endcase
            qbar=~q;
        end
    else
        begin
            q=1'b0;qbar=~q;
        end
    end
endmodule
```

#### **Test bench for SR flipflop:**

```
module tb_sr_flipflop;
reg s,r,clk,rst;
wire q,qbar;
sr_flipflop SR(s,r,clk,rst,q,qbar);
always #50 clk = ~clk;
initial
begin
    clk=1;
    rst=0;
    s=1'b0; r=1'b0;
    #100 s=1'b0; r=1'b1;
    #100 s=1'b1; r=1'b0;
    #100 s=1'b1; r=1'b1;
```

```

        #100 rst=1;
        s=1'b0; r=1'b0;
        #100 s=1'b0; r=1'b1;
        #100 s=1'b1; r=1'b0;
        #100 s=1'b1; r=1'b1;
        #100 $stop;
    end
initial begin
$monitor("At time=%t, clk=%b,rst=%b, s=%b,r=%b,q=%b,qbar=%b",$time,clk,rst,s,r,q,qbar);
    end
endmodule

```

### **JK flipflop:**

```

module jk_flipflop(j,k,clk,rst,q,qbar);
input j,k,clk,rst;
output reg q,qbar;
always @ (posedge clk)
    begin
        if (rst==0)
            begin
                case ({j,k})
                    2'b00: q=q;
                    2'b01: q=1'b0;
                    2'b10: q=1'b1;
                    2'b11: q=~q;
                endcase
                qbar=~q;
            end
        else
            begin
                q=1'b0;qbar=~q;
            end
        end
    end
endmodule

```

### **Test bench for JK flipflop:**

```

module tb_jk_flipflop;
reg j,k,clk,rst;
wire q,qbar;
jk_flipflop jk(j,k,clk,rst,q,qbar);
always #50 clk = ~clk;
initial
    begin
        clk=1;
        rst=0;
        j=1'b0; k=1'b0;
        #100 j=1'b0; k=1'b1;
        #100 j=1'b1; k=1'b0;
        #100 j=1'b1; k=1'b1;
        #100 rst=1;
        j=1'b0; k=1'b0;
        #100 j=1'b0; k=1'b1;
        #100 j=1'b1; k=1'b0;
    end
endmodule

```

```

        #100 j=1'b1; k=1'b1;
        #100 $stop;
    end
initial begin
$monitor("At time=%t, clk=%b,rst=%b, j=%b,k=%b,q=%b,qbar=%b", $time,clk,rst,j,k,q,qbar);
    end
endmodule

```

#### **D flipflop:**

```

module d_flipflop(Q,D,clk,reset,Qbar);
input D,clk,reset;
output reg Q,Qbar;
always @(posedge clk or posedge reset)
begin
    if (reset == 1'b1 )
    begin
        Q = 1'b0;
        Qbar=~Q;
    end
    else
    begin
        Q = D;
        Qbar=~Q;
    end
end
endmodule

```

#### **Test bench for D flipflop:**

```

module tb_d_flipflop;
reg D,clk,reset;
wire Q,Qbar;
d_flipflop DF(Q,D,clk,reset,Qbar);
initial
begin
    clk = 1'b1;
    forever #20 clk = ~clk ;
end
initial
begin
    reset = 1'b0;
    D = 1'b0;
    #40 D = 1'b1;
    #40 reset = 1'b1;
    D = 1'b0;
    #40 D = 1'b1;
    #40 $finish ;
end
initial begin
    $monitor("At time %0t: clk = %b, reset = %b, D = %b, Q = %b, Qbar = %b",
        $time, clk, reset, D, Q, Qbar);
end
endmodule

```

**T flipflop:**


```
module t_flipflop (T,clk,reset,Q,Qbar);
  input T,clk,reset;
  output reg Q,Qbar;
  always @(posedge clk or posedge reset)
  begin
    if (reset) begin
      Q = 1'b0;
      Qbar=~Q;end
    else
      if (T) begin
        Q = ~Q;
        Qbar=~Q; end
      else
        begin
          Q = Q;
          Qbar=~Q; end
        end
      end
endmodule
```

**Test bench for T flipflop:**


```
module tb_t_flipflop;
  reg T;
  reg clk;
  reg reset;
  wire Q,Qbar;
  t_flipflop TF(T,clk,reset,Q,Qbar);
  initial begin
    clk = 0;
    forever #5 clk = ~clk;
  end
  initial begin
    reset = 1; T = 0;
    #15;
    reset = 0;
    T = 1 ;
    #10 T = 0;
    #10 T = 1;
    #10 T = 0;
    #10 $finish;
  end
  initial begin
    $monitor("Time: %0t | T: %b | clk: %b | reset: %b | Q: %b", $time, T, clk, reset, Q);
  end
endmodule
```

SIMULATION WAVEFORM:


SR flipflop:

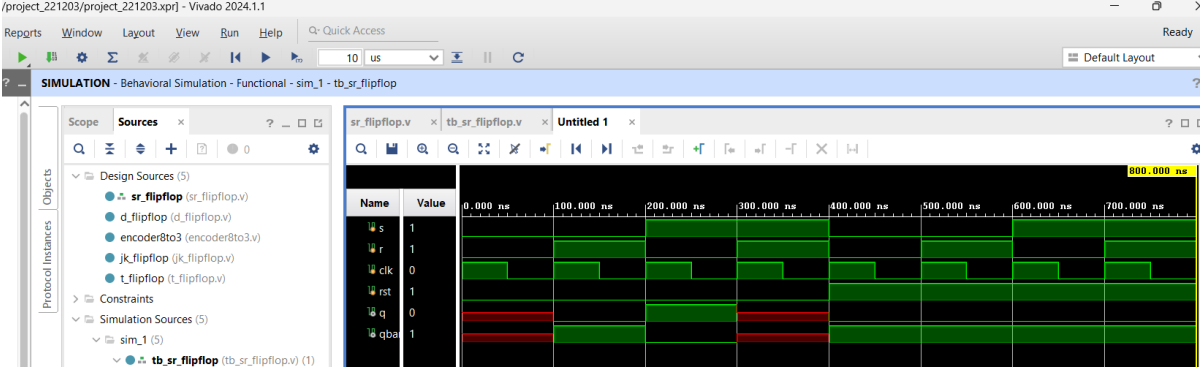


JK flipflop:

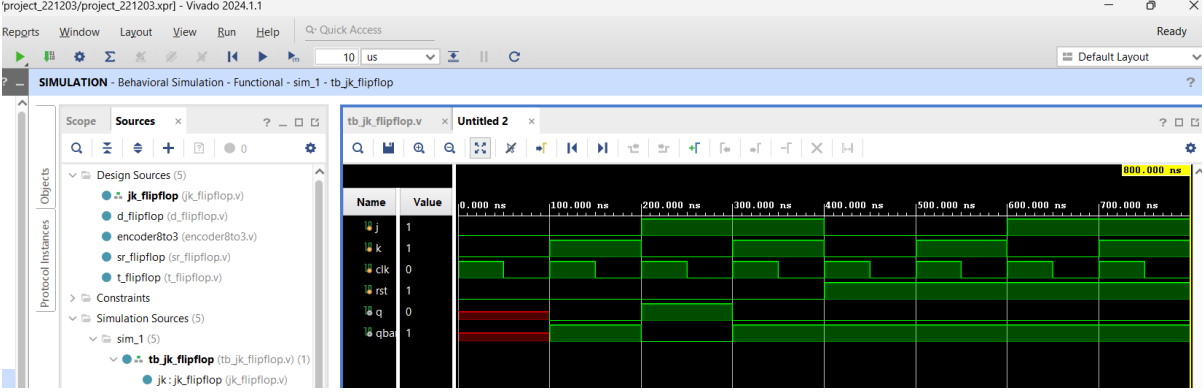

D flipflop:

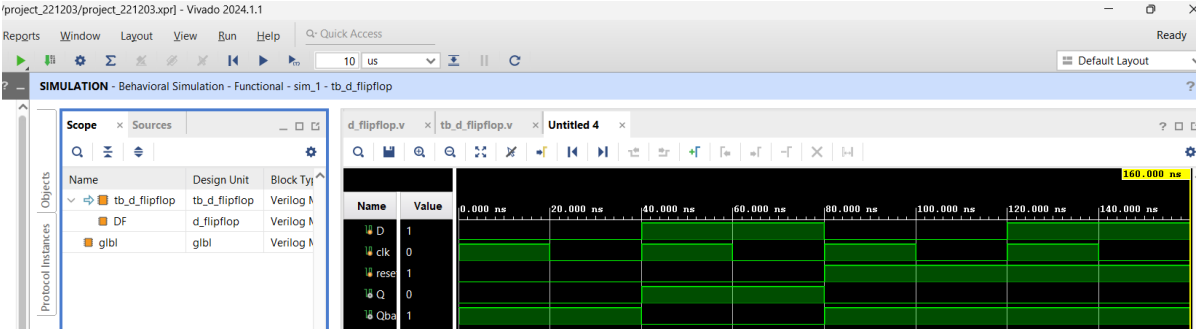

T flipflop:

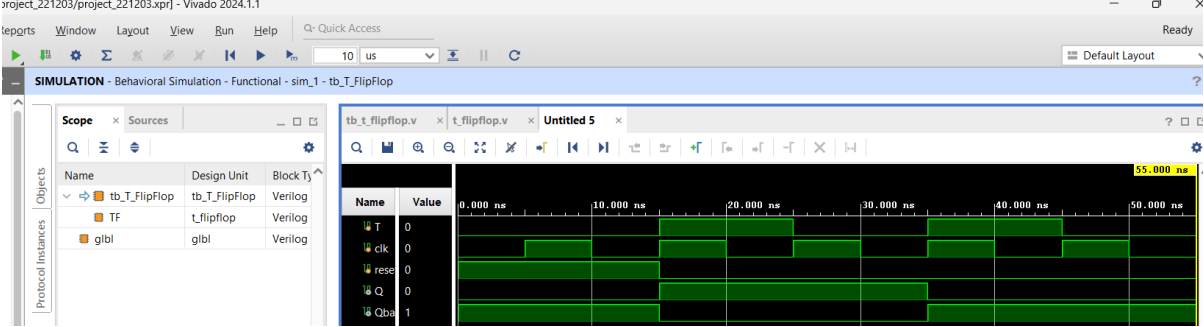

## HADWARE OUTPUT:

### SR flipflop:

S: U1

clk: W5


Q: L1

R: T1

rst: R2

Qbar: P1

For S=1 ,R=0, clk=1, rst=1

 

### JK flipflop:

J: R2

clk: W5


Q: L1

K: T1

rst: U1

Qbar: P1

For J=1 ,K=0, clk=1, rst=0

 



### D flipflop:

D: R2


clk: W5

reset: T1

Q: L1

Qbar: P1

For D=1, clk=1, reset=0

 

### T flipflop:

T: T1


clk: W5

reset: R2

Q: L1


Qbar: P1

For T=1, clk=1, reset=0

 


## TRUTH TABLES AND CIRCUIT DIAGRAMS:

### SR flipflop:

 

INPUTS			OUTPUT	STATE
CLK	S	R	Q	
X	0	0	No Change	Previous
↑	0	1	0	Reset
↑	1	0	1	Set
↑	1	1	-	Forbidden

 



$$Q_{n+1} = S + Q_n R'$$

TRUTH TABLE

S	R	$Q_N$	$Q_{N+1}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-

### JK flipflop:


Trigger	Inputs		Output				Inference
			Present State		Next State		
CLK	J	K	Q	Q'	Q	Q'	
	x	x	-		-		Latched
	0	0	0	1	0	1	No Change
			1	0	1	0	
	0	1	0	1	0	1	Reset
			1	0	0	1	
	1	0	0	1	1	0	Set
			1	0	1	0	
	1	1	0	1	1	0	Toggles
			1	0	0	1	

  

$$Q_{n+1} = JQ_n' + K'Q_n$$




### D flipflop:

 

CLK	D	$Q_n$	$\bar{Q}_n$	Action
0	X	$Q_{n-1}$	$\bar{Q}_{n-1}$	HOLD
1	0	0	1	Reset
1	1	1	0	Set


Input			Output	
D	reset	clock	Q	Q'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	1	0
1	1	0	0	1
1	1	1	0	1

 

$$Q_{n+1} = D$$


### T flipflop:

Symbol

 

Inputs		Outputs	
CLK	T	$Q_{n+1}$	Action
0	X	$Q_n$	No change
1	0	$Q_n$	No change
1	1	$\bar{Q}_n$	Toggle

T	Previous		Next	
	Q	Q'	Q	Q'
0	0	1	0	1
0	1	0	1	0
1	0	1	1	0
1	1	0	0	1

 

$$Q_{n+1} = T \oplus Q_n$$

### RESULT:

Thus, flip-flops were successfully implemented in Verilog HDL and their functionalities were verified through behavioral simulation using Xilinx Vivado software on the Basys3 FPGA board.