

EX. NO: 07

DATE : 24/10/2024

## Comparators, Parity Generator and ALU

**AIM:** To verify the functionalities of Comparators, Parity Generator and ALU using Verilog HDL program.

**SOFTWARE USED:** Xilinx Vivado

**HARDWARE USED:** Basys3 FPGA Board

### **COMPARATOR:**

#### **Verilog HDL Code for 4 bit comparator:**

```
module comparator_4bit(A, B, less, equal, greater);
    input [3:0] A, B;
    output reg less, equal, greater;
    wire less_1, equal_1, greater_1;
    wire less_0, equal_0, greater_0;
    comparator comp1(
        .A(A[1:0]),
        .B(B[1:0]),
        .less_0,
        .equal_0,
        .greater_0
    );
    comparator comp2(
        .A(A[3:2]),
        .B(B[3:2]),
        .less_1,
        .equal_1,
        .greater_1
    );
    always @(*) begin
        if (A[3:2] > B[3:2]) begin
            less = 0; equal = 0; greater = 1;end
        else if (A[3:2] < B[3:2]) begin
            less = 1; equal = 0; greater = 0;end
        else begin
            less = less_0;
            equal = equal_0;
            greater = greater_0;
        end
    end
endmodule

module comparator(A,B, less, equal, greater);
    input [1:0]A,B;
```

```

        output reg less, equal, greater;
always@(A or B)
    begin
        if (A>B)
            begin
                less = 0;equal = 0;greater = 1 ;
            end
        else if (A<B)
            begin
                less = 1;equal = 0;greater = 0 ;
            end
        else
            begin
                less = 0;equal = 1;greater = 0 ;
            end
    end
end
endmodule

```


### **Test bench for 4 bit Comparator:**

```

module tb_comparator;
    reg [3:0] A, B;
    wire less, equal, greater;
    comparator_4bit comp(
        .A(A),
        .B(B),
        .less(less),
        .equal(equal),
        .greater(greater)
    );
    initial begin
        A = 4'b0010; B = 4'b0011; #10;
        A = 4'b0100; B = 4'b0011; #10;
        A = 4'b0011; B = 4'b0011; #10;
        A = 4'b0001; B = 4'b0010; #10;
        A = 4'b1010; B = 4'b0100; #10;
        A = 4'b1111; B = 4'b1111; #10;
        $finish;
    end
    initial begin
        $monitor("A = %b, B = %b -> less: %b, equal: %b, greater: %b", A, B, less,
        equal, greater);
    end
endmodule

```

## SIMULATION WAVEFORM:

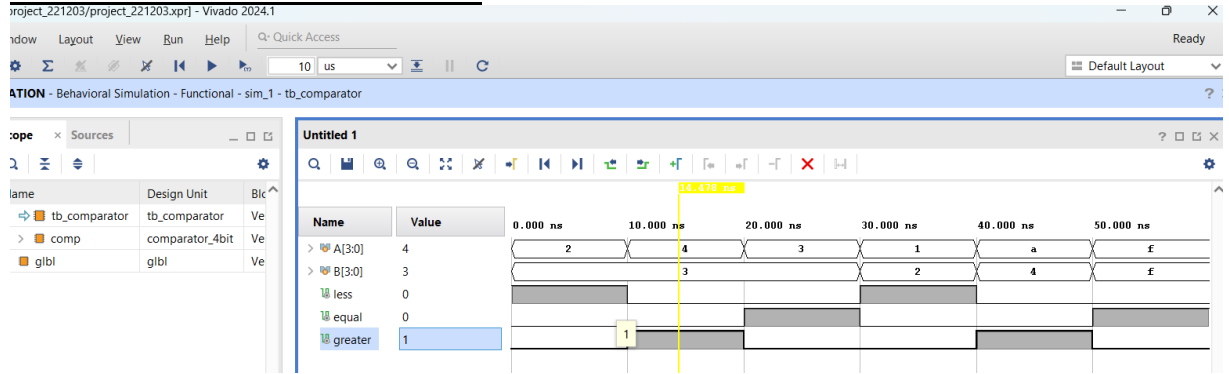

## HARDWARE OUTPUT:

### I/O ports:

#### **Inputs:**

A[3]: R2  
A[2]: T1  
A[1]: U1  
A[0]: W2

B[3]: W17  
B[2]: W16  
B[1]: V16  
B[0]: V17

#### **Outputs:**


equal: P1  
less: L1  
greater: N3

#### **For**

A[3]=0, A[2]= 1, A[1]=1, A[0]=0  
B[3]=0, B[2]= 1, B[1]=1, B[0]=0

#### **Output:**


equal=1, less=0, greater=0

 

### TRUTH TABLE FOR 2 BIT COMARATOR:

A	B	Less	Greater	Equal
00	00	0	0	1
00	01	1	0	0
00	10	1	0	0
00	11	1	0	0
01	00	0	1	0
01	01	0	0	1
01	10	1	0	0
01	11	1	0	0
10	00	0	1	0
10	01	0	1	0
10	10	0	0	1
10	11	1	0	0
11	00	0	1	0
11	01	0	1	0
11	10	0	1	0
11	11	0	0	1

### BLOCK DIAGRAM:

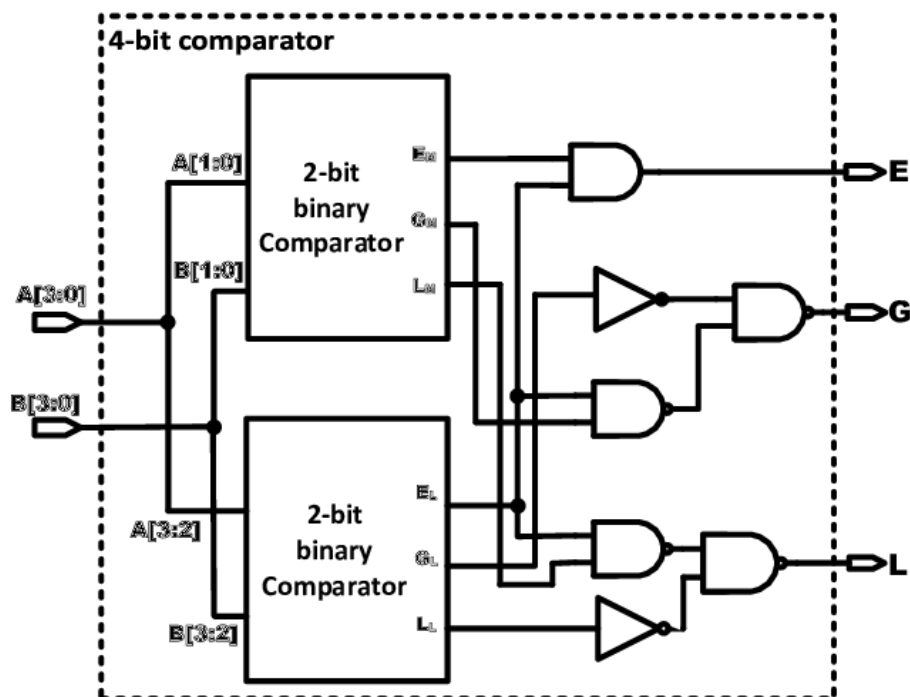

**Fig. 3:** The architecture for 4-bit binary comparator using a 2-bit elementary binary comparator.

## PARITY GENERATOR:

### Verilog HDL Code:

```

module evenparitygenerator(d, evenparity);
input [7:0]d;
output reg evenparity;
always@(d)
    begin
        evenparity ^= d;
    end
endmodule

```


### Test bench for Parity Generator:

```

module tb_evenparitygenerator;
reg [7:0]d;
wire evenparity;
evenparitygenerator EVEN(d, evenparity);
initial
    begin
        d=8'b00000000;
        #100 d=8'b01110110;
        #100 d=8'b00011110;
        #100 d=8'b11111010;
        #100 d=8'b00110000;
        #100 d=8'b00100101;
        #100 $finish;
    end
initial begin
$monitor("Time: %0t |d: %b | evenparity: %b", $time,d,evenparity);
end
endmodule

```

### SIMULATION WAVEFORM:

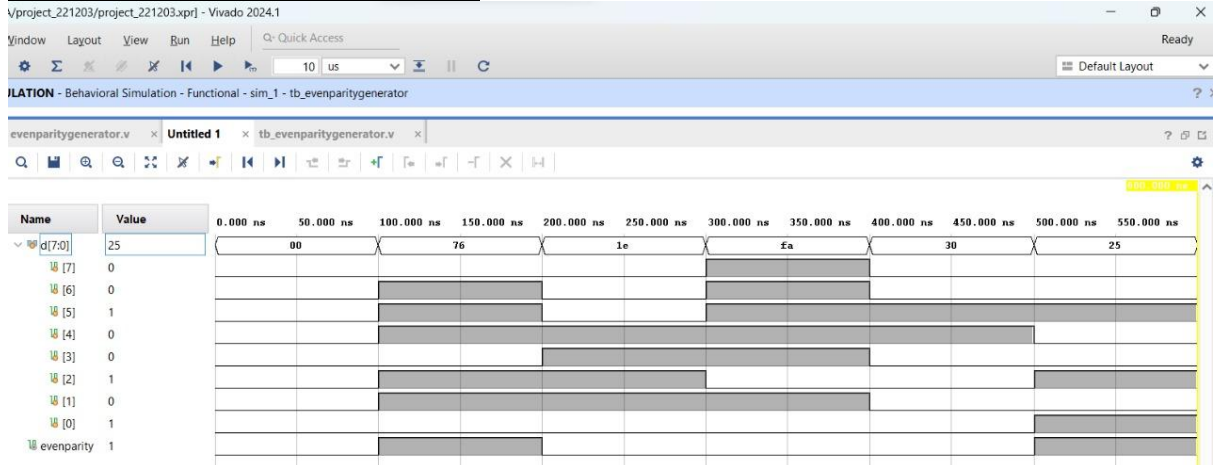

## HARDWARE OUTPUT:

### I/O ports:

#### Inputs:

d[7]: R2

d[6]: T1

d[5]: U1

d[4]: W2

d[3]: R3

d[2]: T2

d[1]: T3

d[0]: V2

#### Outputs:


evenparity: L1

### For

d[7]=0, d[6]= 1, d[5]=1, d[4]=0

d[3]=0, d[2]= 1, d[1]=1, d[0]=0

output: evenparity= 1

 

### **TRUTH TABLE:**

#### **Parity Generator: even**

A	B	C	Paritybit
0	0	0	0
0	0	1	1
0	1	1	0

### **CIRCUIT DIAGRAM:**

 


Fig. even parity generator

## **ALU:**

### **Verilog HDL Code:**

```
module ALU (  
    input [2:0] A,  
    input [2:0] B,  
    input [3:0] opcode,  
    output reg [2:0] ALU_out,  
    output reg Zero  
);  
always @(*) begin  
    case (opcode)  
        4'b0000: ALU_out = A + B;  
        4'b0001: ALU_out = A - B;  
        4'b0010: ALU_out = A * B;  
        4'b0011: ALU_out = A / B;  
        4'b0100: ALU_out = A << B;  
        4'b0101: ALU_out = A >> B;  
        4'b0110: ALU_out = A << 1;  
        4'b0111: ALU_out = {A[0], A[2:1]};  
        4'b1000: ALU_out = A & B;  
        4'b1001: ALU_out = A | B;  
        4'b1010: ALU_out = A ^ B;  
        4'b1011: ALU_out = ~(A & B);  
        4'b1100: ALU_out = ~(A ^ B);  
        4'b1101: ALU_out = (A > B) ? 1 : 0;  
        4'b1110: ALU_out = (A < B) ? 1 : 0;  
        4'b1111: ALU_out = (A == B) ? 1 : 0;  
        default: ALU_out = 3'b0;  
    endcase  
    Zero = (ALU_out == 3'b0) ? 1 : 0;  
end  
endmodule
```

### **Test bench for ALU:**

```
module tb_ALU;  
    reg [2:0] A;  
    reg [2:0] B;  
    reg [3:0] opcode;  
    wire [2:0] ALU_out;  
    wire Zero;  
    ALU alu(  
        .A(A),  
        .B(B),  
        .opcode(opcode),  
        .ALU_out(ALU_out),  
        .Zero(Zero)
```




```

        .Zero(Zero)
    );
initial begin
    A = 3'b101; B = 3'b111;
    opcode = 4'b0000; #10
    opcode = 4'b0001; #10
    opcode = 4'b0010; #10
    opcode = 4'b0011; #10
    opcode = 4'b0100; #10
    opcode = 4'b0101; #10
    opcode = 4'b0110; #10
    opcode = 4'b0111; #10
    opcode = 4'b1000; #10
    opcode = 4'b1001; #10
    opcode = 4'b1010; #10
    opcode = 4'b1011; #10
    opcode = 4'b1100; #10
    opcode = 4'b1101; #10
    opcode = 4'b1110; #10
    opcode = 4'b1111; #10
    $stop;
end
initial begin
    $monitor("Time: %0t | A: %b | B: %b | Opcode: %b | ALU_out: %b | Zero: %b", $time, A, B, opcode, ALU_out, Zero);

end
endmodule

```

## SIMULATION WAVEFORM:

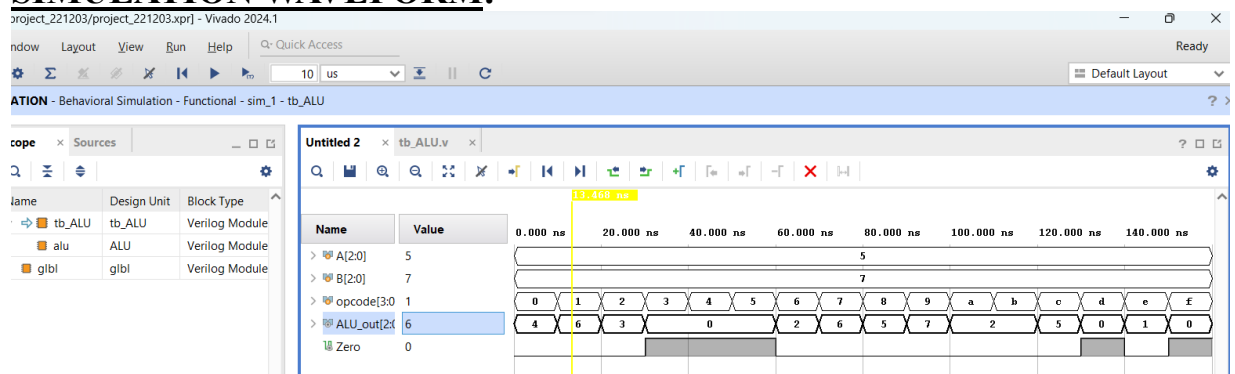

## HARDWARE OUTPUT:

### I/O ports:

#### **Inputs:**

A[2]: R2  
A[1]: T1  
A[0]: U1  
B[2]: W2  
B[1]: R3  
B[0]: T2

opcode [3]: W17  
opcode [2]: W16  
opcode [1]: V16  
opcode [0]: V17

#### **Outputs:**


ALU\_out [3]: L1  
ALU\_out [2]: P1  
ALU\_out [1]: N3  
ALU\_out [0]:  
Zero: U16

For


opcode=0110 , A = 0100 , B =0000

Output:

ALU\_out= 1000 (A<<1) i.e. A= 1000

 

## BLOCK DIAGRAM:

 

### **RESULT:**

The Comparators, Parity Generator and ALU has been successfully designed and implemented using Verilog HDL, and their functionalities have been thoroughly verified through simulation with Xilinx Vivado software on the Basys3 FPGA board.