

EX. NO: 01

DATE :

## ADDERS AND SUBTRACTORS

**AIM:** To simulate Adders and Subtractors in behavior, structural, and dataflow model of Verilog HDL.

**SOFTWARE USED:** Xilinx Vivado

**HARDWARE USED:** Basys3 FPGA Board

### **ADDERS:**

#### **VERILOG HDL CODE:**

##### **Half Adder in Behavioral model:**

```
module half_adder_behav (S,C,A,B);
input A,B;
output S,C;
reg S,C;
always@(A or B)
begin
if(A==0 && B==0)
begin S=0;C=0; end
else if(A==0 && B==1)
begin S=1;C=0; end
else if(A==1 && B==0)
begin S=1;C=0; end
else
begin S=0;C=1; end
end
endmodule
```

##### **Half Adder in Structural model:**

```
module half_adder_struct(S,C,A,B);
input A, B;
output S, C;
xor (S,A,B);
and (C,A,B);
endmodule
```

##### **Half Adder in Data flow model:**

```
module half_adder_data(S,C,A,B);
input A,B;
output S,C;
assign S=A ^ B;
assign C= A & B;
endmodule
```

**Half Adder Test bench:**

```
module half_adder_test;
reg A,B;
wire S,C;
//half_adder_behav HA1(S,C,A,B);
//half_adder_data HA2(S,C,A,B);
half_adder_struct HA3(S,C,A,B);
initial
begin
    A=0;    B = 0;
#10  A = 0;    B = 1;
#10  A = 1;    B = 0;
#10  A = 1;    B = 1;
#10 $stop;
$monitor ("A=%b, B=%b, C=%b, S=%b", A, B, C, S);
end
endmodule
```

**Full Adder in Behavioral model:**

```
module full_adder_behav(a,b,c,sum,carry);
input a,b,c;
output sum ,carry;
reg sum,carry;
always @(a or b or c)
begin
if (a==0 && b==0 && c==0)
begin sum=0;carry=0; end
else if(a==0 && b==0 && c==1)
begin sum=1;carry=0;end
else if(a==0 && b==1 && c==0)
begin sum=1;carry=0;end
else if(a==0 && b==1 && c==1)
begin sum=0;carry=1;end
else if(a==1 && b==0 && c==0)
begin sum=1;carry=0;end
else if(a==1 && b==0 && c==1)
begin sum=0;carry=1;end
else if(a==1 && b==1 && c==0)
begin sum=0;carry=1;end
else
begin sum=1;carry=1;end
end
endmodule
```

**Full Adder in Structural model:**

```
module full_adder_structural(a,b,c,sum,carry);
input a,b,c;
output sum,carry;
wire s1,c1,c2;
halfadder HA1(a,b,s1,c1);
halfadder HA2(s1,c,sum,c2);
or(carry,c1,c2);
endmodule
```

```
module halfadder (A, B,Sum,Carry);
input A, B;
output Sum, Carry;
xor (Sum,A,B);
and (Carry,A,B);
endmodule
```

**Full Adder in Data flow model:**

```
module full_adder_data(a,b,c,sum,carry);
input a,b,c;
output sum,carry;
assign sum=a^b^c;
assign carry =(a&b)|(b&c)|(c&a);
endmodule
```

**Test bench for Full Adder:**

```
module full_adder_test;
reg a,b,c;
wire sum, carry;
full_adder_structural FA1(a,b,c,sum,carry);
//full_adder_behav FA2(a,b,c,sum,carry);
//full_adder_data FA3(a,b,c,sum,carry);
initial
begin
a=0;b=0;c=0;
#10 a=0;b=0;c=1;
#10 a=0;b=1;c=0;
#10 a=0;b=1;c=1;
#10 a=1;b=0;c=0;
#10 a=1;b=0;c=1;
#10 a=1;b=1;c=0;
#10 a=1;b=1;c=1;
#10 $stop;
$monitor("a=%b,b=%b,c=%b,sum=%b,carry=%b",a,b,c,sum,carry);
end
endmodule
```

#### **4-Bit Parallel Adder(Ripple Carry Adder):**

```
module full_adder (a,b,c,sum,carry);
input a,b,c;
output sum,carry;
assign sum=a^b^c;
assign carry =(a&b)|(b&c)|(c&a);
endmodule


module RCA(a,b,c,sum, carry);
input [3:0]a,b;
input c;
output [3:0]sum;
output carry;
wire c1,c2,c3;
full_adder fa1(a[0],b[0],c,sum[0], c1);
full_adder fa2(a[1],b[1],c1,sum[1], c2);
full_adder fa3(a[2],b[2],c2,sum[2], c3);
full_adder fa4(a[3],b[3],c3,sum[3], carry);
endmodule
```

#### **Test bench for 4-Bit Parallel Adder:**


```
module RCA_test;
reg [3:0]a,b;
reg c;
wire [3:0]sum;
wire carry;
RCA full_adder(a,b,c,sum, carry);
initial
begin
$monitor("%d a=%b, b=%b, c=%b, sum=%b, carry=%b", $time, a, b, c, sum, carry);
a = 4'b1001; b = 4'b1100; c = 1; //3
#100 a = 4'b0001; b = 4'b1111; c = 1; // 31
#100 a = 4'b0011; b = 4'b1011; c = 0; // 59
#100 a = 4'b0101; b = 4'b0111; c = 1; // 87
#100 a = 4'b0111; b = 4'b0011; c = 0; // 115
#100 a = 4'b1000; b = 4'b1111; c = 1; // 143
#100 a = 4'b1010; b = 4'b1011; c = 0; // 171
#100 a = 4'b1100; b = 4'b0111; c = 1; // 199
end
endmodule
```

## SIMULATION WAVEFORM:


### Half Adder in Behavioral model:

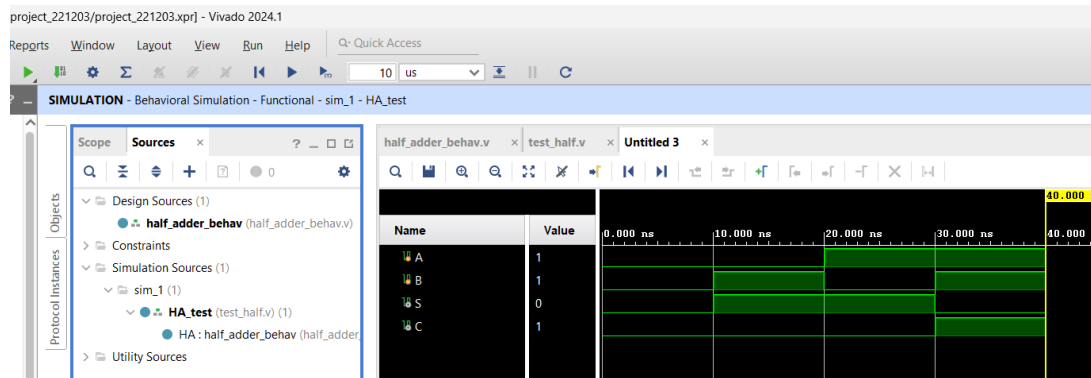


### Half Adder in Structural model:

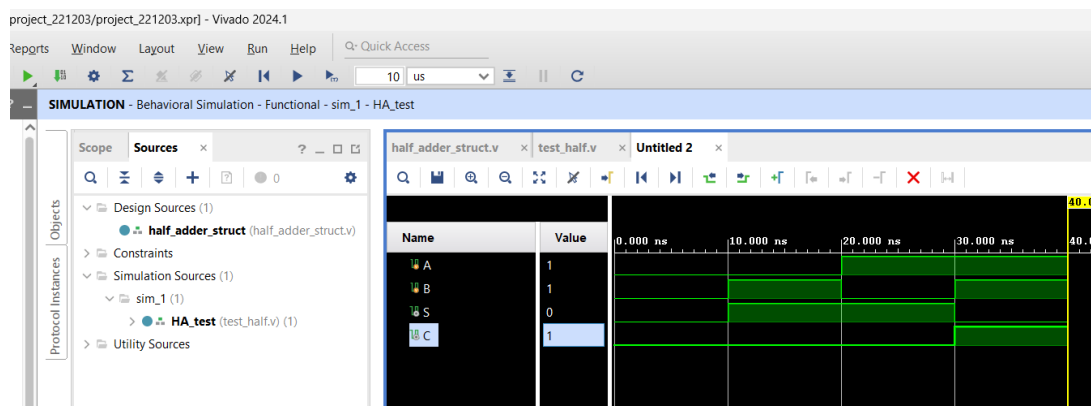


### Half Adder in Data flow model:

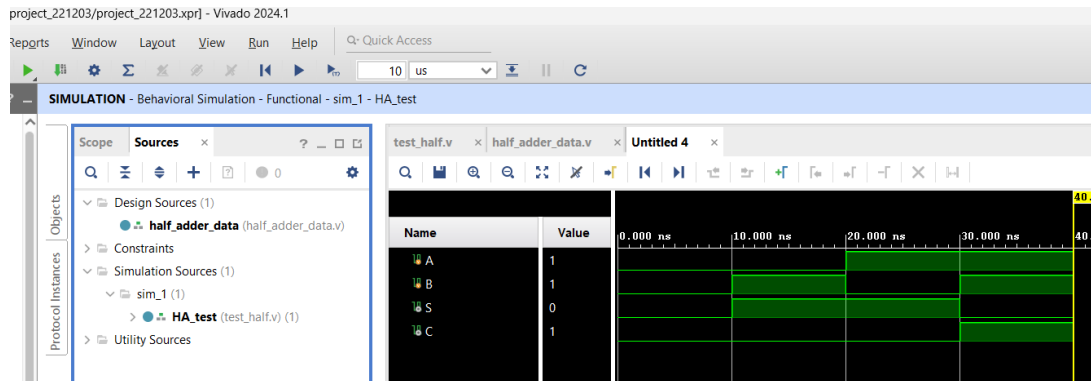


### Full Adder in Behavioral model:

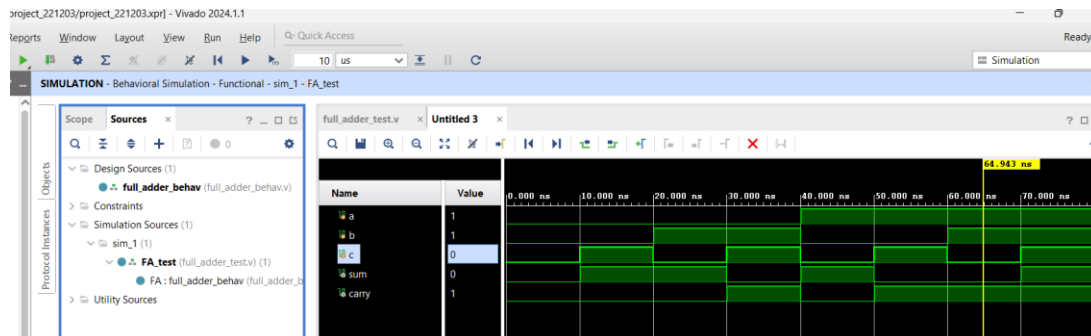


## Full Adder in Structural model:

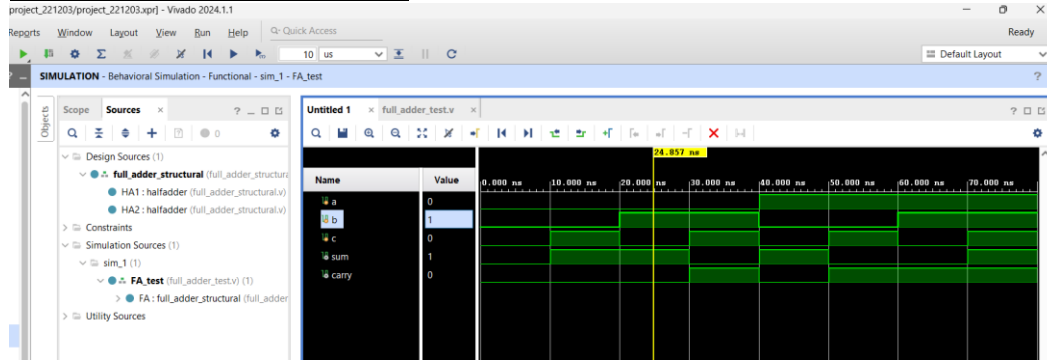

## Full Adder in Data flow model:

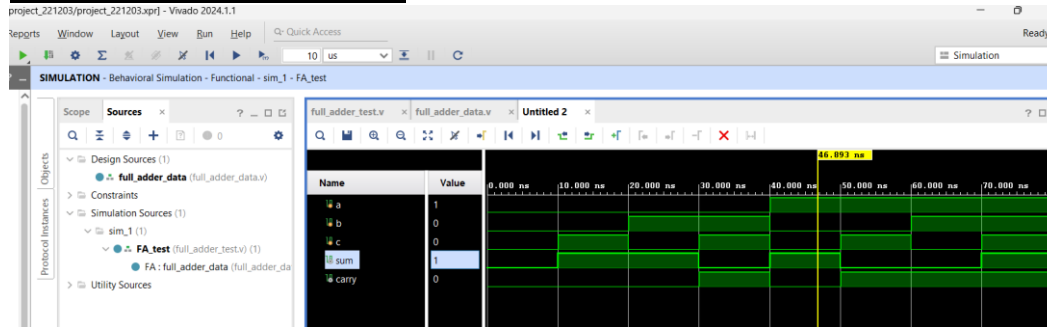
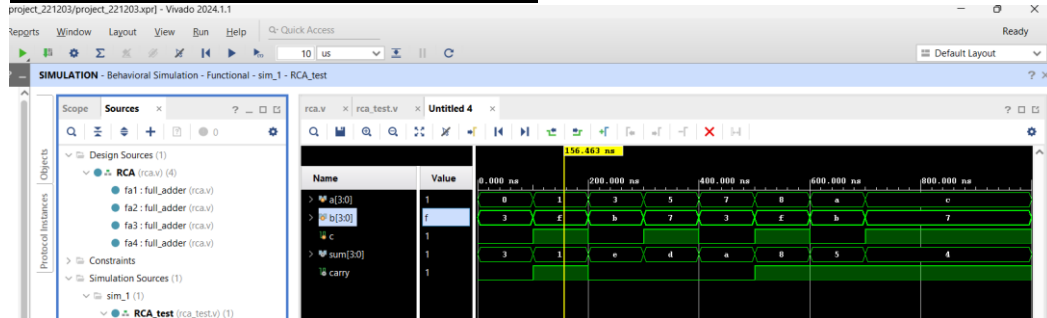
## 4-Bit Parallel Adder(Ripple Carry Adder):



## HADWARE OUTPUT:

### Half Adder:

#### I/O ports:


A: R2

B: T1

CARRY: L1

SUM : P1

For A=1, B=1

 



### Full Adder:

#### I/O ports:

a: R2


carry: P1

b: T1

sum : L1

c: U1

For A=1, B=0, C=1

 

### 4-Bit Parallel Adder(Ripple Carry Adder):

#### I/O ports:

a[3]: R2

b[3]: W17

sum[3]: L1

a[2]: T1

b[2]: W16

sum[2]: P1

a[1]: U1

b[1]: V16

sum[1]: N3

a[0]: W2

b[0]: V17

sum[0]: P3


Cin : R3

Cout : U3

For a[3]=0, a[2]=0, a[1]=0, a[0]=1

b[3]=1, b[2]=1, b[1]=1, b[0]=1

Cin=1

 

## TRUTH TABLE:

### Half Adder:

Input		Output	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$\text{Sum} = A'B + AB' = A \oplus B$$

$$\text{Carry} = AB$$

### Full Adder:


Input			Output	
A	B	Cin	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\text{Sum} = A \oplus B \oplus \text{Cin}$$


$$\text{Carry} = (AB) + \text{Cin}A \oplus \text{Cin}B$$

## CIRCUIT DIAGRAMS:

### Half Adder:

 


### Full Adder:

 



#### 4-Bit Parallel Adder:

 

#### SUBTRACTORS:

##### VERILOG HDL CODE:

###### Half Subtractor in Behavioral model:

```
module
half_subtractor_behav(a,b,diff,borrow);
input a, b;
output diff, borrow;
reg diff, borrow;
always @(a or b)
begin
if (a == 0 && b == 0)
begin diff = 0; borrow = 0; end
else if (a == 0 && b == 1)
begin diff = 1; borrow = 1; end
else if (a == 1 && b == 0)
begin diff = 1; borrow = 0; end
else if (a == 1 && b == 1)
begin diff = 0; borrow = 0; end
end
endmodule
```

###### Half Subtractor in Structural model:

```
module
half_subtractor_struct(a,b,differ,borrow);
input a,b;
output differ,borrow;
wire x;
xor (differ,a,b);
not (x,a);
and (borrow,x,b);
endmodule
```

###### Half Subtractor in Data flow model:

```
module
half_subtractor_data(a,b,differ,borrow);
input a,b;
output differ,borrow;
assign differ=a^b;
assign borrow=(~a)&b;
endmodule
```

###### Test bench for Half Subtractor:

```
module half_subtractor_test;
reg A,B;
wire DIFFER,BORROW;
half_subtractor_behav HS1(A,B,DIFFER,BORROW);
//half_subtractor_struct HS2(A,B,DIFFER,BORROW);
//half_subtractor_data HS3(A,B,DIFFER,BORROW);
initial
begin
A = 0; B = 0;
#10 A = 0; B = 1;
#10 A = 1; B = 0;
#10 A = 1; B = 1;
#10 $stop;
$monitor ("A=%b, B=%b, DIFFER=%b, BORROW=%b", A, B, DIFFER, BORROW);
end
endmodule
```

**Full Subtractor in Behavioral model:**

```
module full_subtractor_behav(a,b,c,differ,borrow);
input a,b,c;
output reg differ,borrow;
always @(a or b or c)
begin
if (a==0 && b==0 && c==0)
begin differ=0; borrow=0; end
else if (a==0 && b==0 && c==1)
begin differ=1; borrow=1; end
else if (a==0 && b==1 && c==0)
begin differ=1; borrow=1; end
else if (a==0 && b==1 && c==1)
begin differ=0; borrow=1; end
else if (a==1 && b==0 && c==0)
begin differ=1; borrow=0; end
else if (a==1 && b==0 && c==1)
begin differ=0; borrow=0; end
else if (a==1 && b==1 && c==0)
begin differ=0; borrow=0; end
else
begin differ=1; borrow=1; end
end
endmodule
```

**Full Subtractor in Structural model:**

```
module half_subtractor_struct(a,b,differ,borrow);
input a,b;
output differ,borrow;
wire x;
xor (differ,a,b);
not (x,a);
and (borrow,x,b);
endmodule
```

```
module full_subtractor_struct(a,b,c,differ,borrow);
input a,b,c;
output differ,borrow;
wire X,Y,Z;
half_subtractor_struct HS1(a,b,X,Y);
half_subtractor_struct HS2(X,c,differ,Z);
or (borrow,Z,Y);
endmodule
```

**Full Subtractor in Data flow model:**

```
module full_subtractor_dataflow(a,b,c,differ,borrow );
input a,b,c;
output differ,borrow;
assign differ=(a^b^c);
assign borrow=(c&(~(a^b))|((~a)&b);
endmodule
```

#### **Test Bench for Full Subtractor:**

```
module full_subtractor_test;
reg a,b,c;
wire differ,borrow;
full_subtractor_struct FS1(a,b,c,differ,borrow);
//full_subtractor_dataflow FS2(a,b,c,differ,borrow );
//full_subtractor_behav FS3(a,b,c,differ,borrow);
initial
begin
a=0;b=0;c=0;
#10 a=0;b=0;c=1;
#10 a=0;b=1;c=0;
#10 a=0;b=1;c=1;
#10 a=1;b=0;c=0;
#10 a=1;b=0;c=1;
#10 a=1;b=1;c=0;
#10 a=1;b=1;c=1;
#10 $stop;
$monitor("a=%b,b=%b,c=%b,differ=%b,borrow=%b",a,b,c,differ,borrow);
end
endmodule
```

#### **4-Bit Parallel Subtractor:**

```
module four_bit_parallel_subtractor(a,b,c,differ,borrow);
input [3:0] a,b;
input c;
output [3:0] differ;
output borrow;
wire b1,b2,b3;
full_subtractor_data HS1(a[0],b[0],c,differ[0], b1);
full_subtractor_data HS2(a[1],b[1],b1,differ[1], b2);
full_subtractor_data HS3(a[2],b[2],b2,differ[2], b3);
full_subtractor_data HS4(a[3],b[3],b3,differ[3], borrow);
endmodule
```


```
module full_subtractor_data(a,b,c,differ,borrow);
input a,b,c;
output differ,borrow;
assign differ = a ^ b ^ c;
assign borrow = (c & (~a ^ b)) | ((~a) & b);
endmodule
```

### Test Bench for 4-Bit Parallel Subtractor:


```
module FOUR_BIT_SUB_TEST;
reg [3:0] a,b;
reg c;
wire [3:0] differ;
wire borrow;
four_bit_parallel_subtractor HS(a,b,c,differ, borrow);
initial begin
    a = 4'b0000; b = 4'b0011; c = 0;
#100 a = 4'b0001; b = 4'b1111; c = 1;
#100 a = 4'b0011; b = 4'b1011; c = 0;
#100 a = 4'b0101; b = 4'b0111; c = 1;
#100 a = 4'b0111; b = 4'b0011; c = 0;
#100 a = 4'b1000; b = 4'b1111; c = 1;
#100 a = 4'b1010; b = 4'b1011; c = 0;
#100 a = 4'b1100; b = 4'b0111; c = 1;
$monitor("%d a=%b, b=%b, c=%b, differ=%b, borrow=%b", $time, a, b, c, differ, borrow);
end
endmodule
```

### SIMULATION WAVEFORMS:
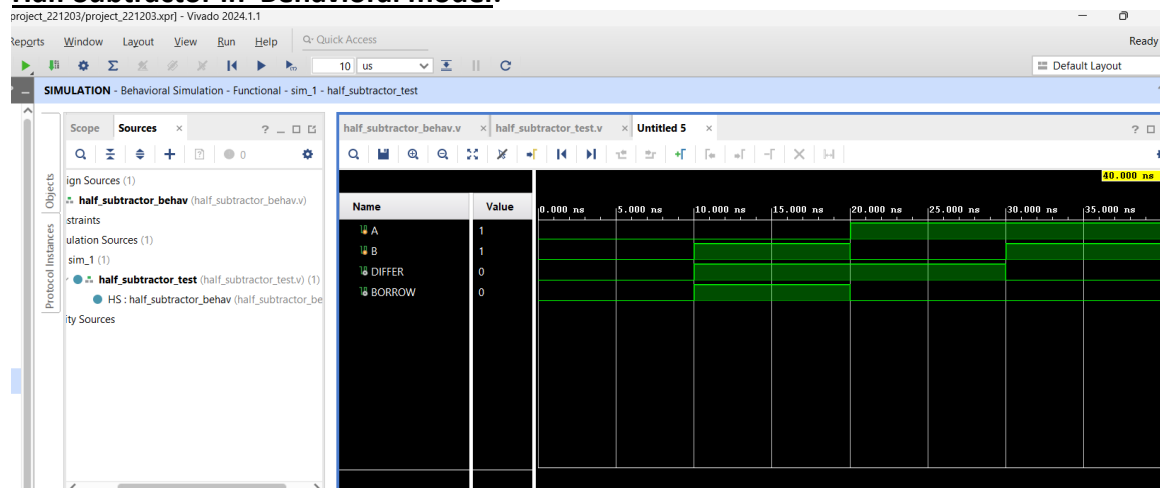
#### Half Subtractor in Behavioral model:



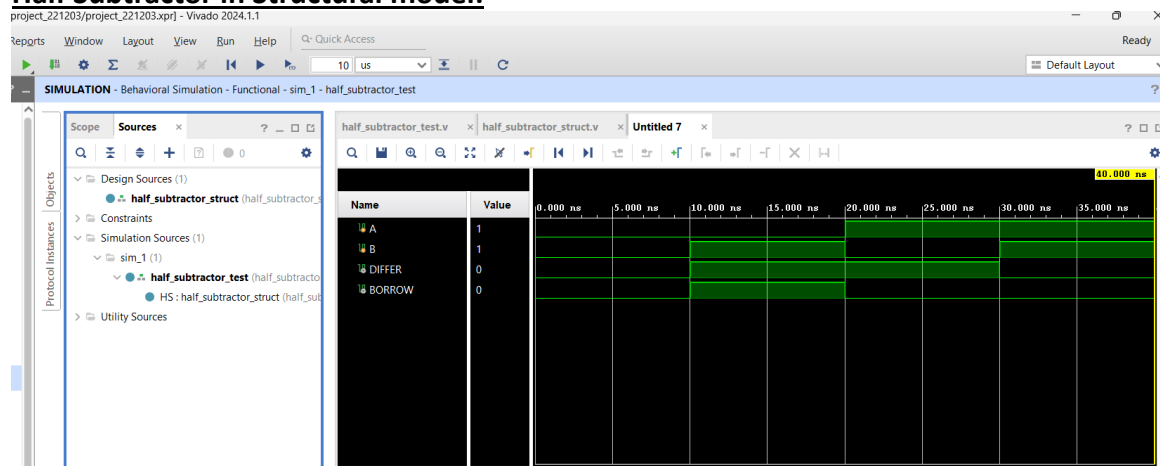
#### Half Subtractor in Structural model:





## 4-Bit Parallel Subtractor:

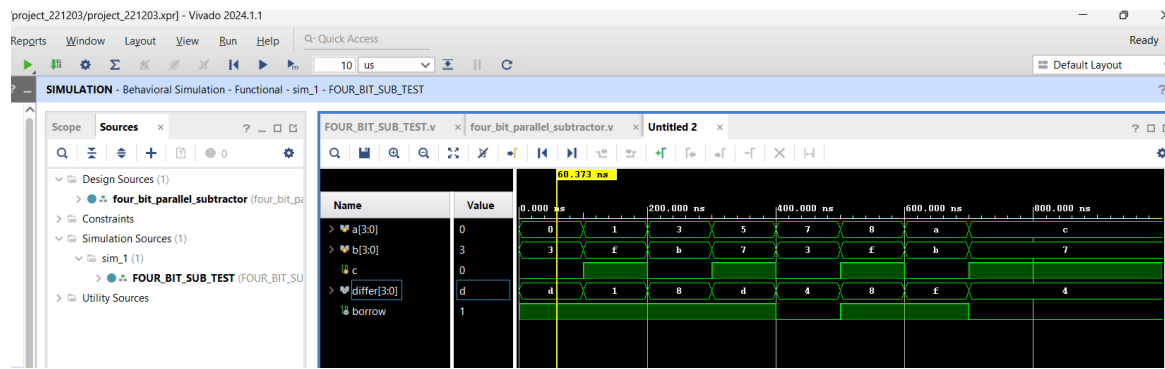

## HADWARE OUTPUT:

### Half Subtractor:

#### I/O ports:


a: R2

b: T1

differ : L1

borrow: P1

For A=0, B=1

 



### Full Subtractor:

#### I/O ports:

a: R2


differ : L1

b: T1

borrow: P1

c: U1

For A=0, B=1, C=0

 

### 4-Bit Parallel Subtractor:

#### I/O ports:

a[3]: R2

b[3]: W17

sum[3]: L1

a[2]: T1

b[2]: W16

sum[2]: P1

a[1]: U1

b[1]: V16

sum[1]: N3

a[0]: W2

b[0]: V17

sum[0]: P3


c(borrow in): R3

borrow(out): U3

For a[3]=0, a[2]=0, a[1]=1, a[0]=1

b[3]=1, b[2]=0, b[1]=1, b[0]=1

borrow in=0

 



### TRUTH TABLE:

#### Half Subtractor:

Inputs		Outputs	
A	B	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$\text{DIFFERENCE} = A \oplus B$$

$$\text{BORROW} = A' B$$

#### Full Subtractor:


A	B	$B_{in}$	D	$B_{out}$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$D = A \oplus B \oplus B_{in}$$


$$B_{out} = A' B_{in} + A' B + B B_{in}$$

### CIRCUIT DIAGRAM:


#### Half Subtractor:

 

#### Full Subtractor:

 

#### 4-Bit Parallel Subtractor:

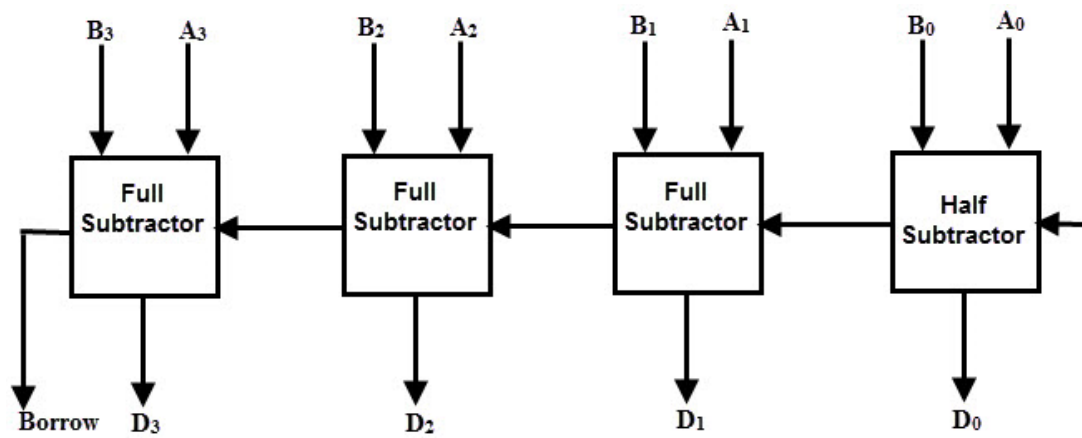

#### RESULT:

Thus the logic circuits for the adders and subtractors are designed in Verilog HDL and the output combinations are verified using Xilinx Vivado software on the Basys3 FPGA board.